

IAT 884 Workshop
Basic Electronics

Basic Concepts

Voltage = Electrical Potential

The volt is the unit measure of electrical pressure.

Amps = Current

Current is the measure of the flow of electrons passing through a given point in a circuit in a given amount of time

Ohms (Ω) = Resistance

Resistance is the measure of a device's opposition to the flow of electrical current.

Watts = Power

Power is a measure of the amount of work that is being done at a given point in time. To calculate power use the formula:


Watts = Volts * Amps

A Simple Water Analogy

Voltage = Water Pressure

Amps = Current Flow


Ohms = Valve

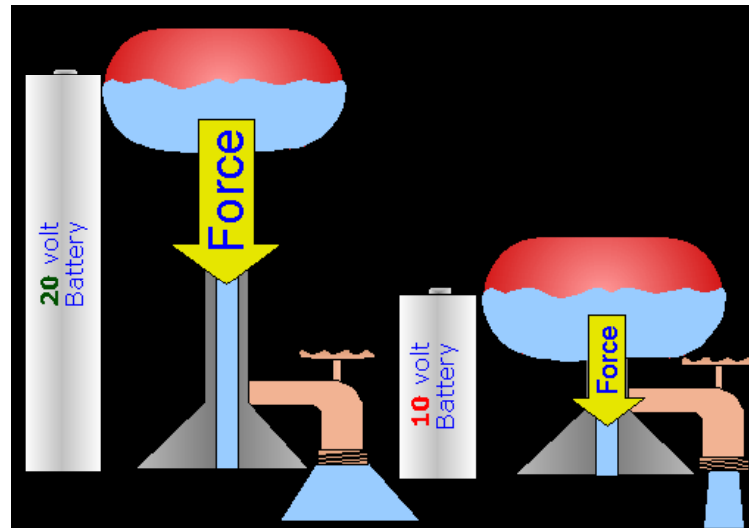

The Flow of Electricity


Conventional Flow:

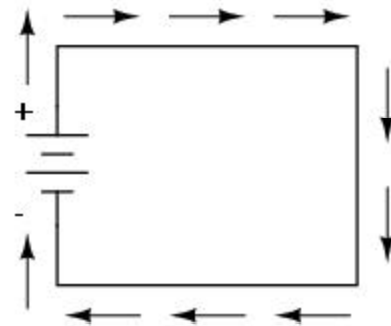Current is viewed as flowing from positive (+) to negative (-) terminals. This is how engineers talk about electricity.



Electron Flow:

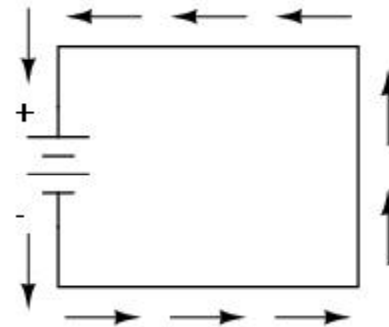In actuality, current flows from negative to positive. It is the movement of electrons from high density to low density.




AC vs. DC Current

Alternating Current:

An electrical current whose magnitude and direction vary cyclically. This is the power we plug things into at home.

Direct Current:

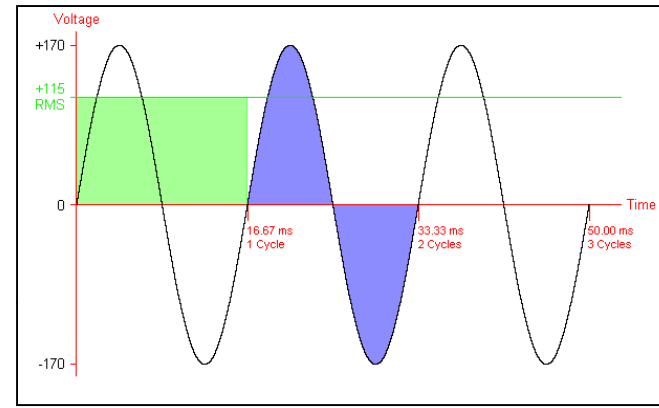An electrical current in which the electric charges flow in the same direction. The kind of current produced by batteries.



AC Current

Common Components

Breadboard: Simple way to connect components without using solder.

Wire: Passes current from one part of a circuit to another.

Power Supply: Supplies electrical energy.

Switch: An on-off switch allows current to flow only when it is closed (on).

Resistor (and Variable Resistor): Restricts the flow of current.

Capacitor: Stores electric charge.

Diode (General Purpose): Only allows current to flow in one direction.

LED (Light Emitting Diode): A transducer that converts electrical energy to light.


Transistor: Can be used as a switch or amplifier.

Relay: A switch that is controlled by another electrical circuit.

Voltage Regulators: Convert a higher voltage into a lower usable voltage

Series Circuit

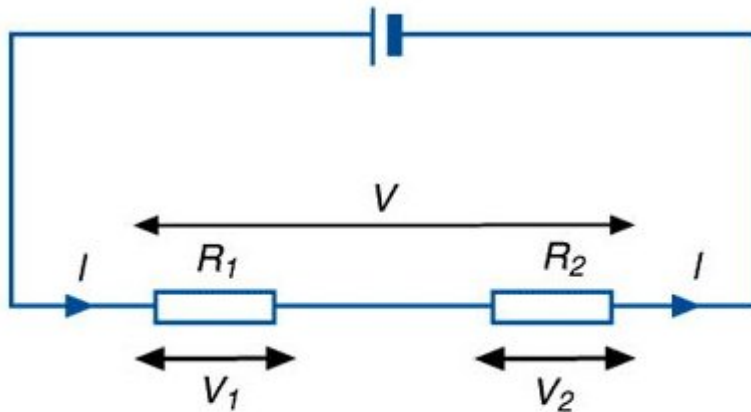An electrical circuit in which the components are connected end to end, so that the current flows through them all one after the other.



Voltage:

$$V_T = V_1 + V_2$$








Resistance:

$$R_T = R_1 + R_2$$

Current:


$$I_T = I_1 = I_2$$

Schematic Symbols

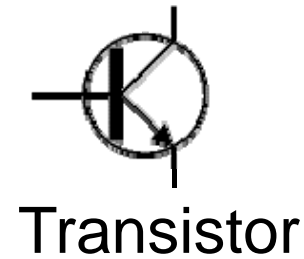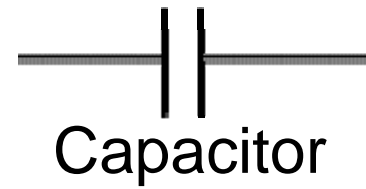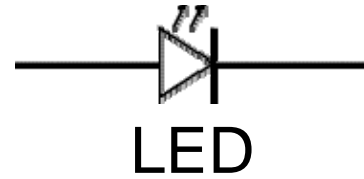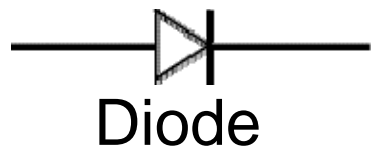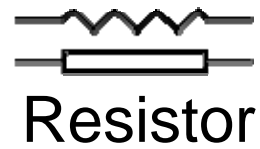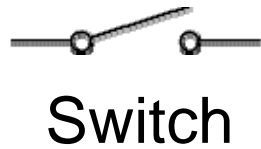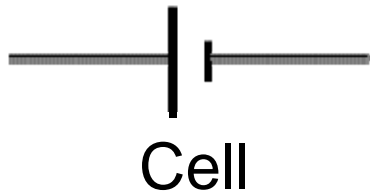

Parallel Circuit

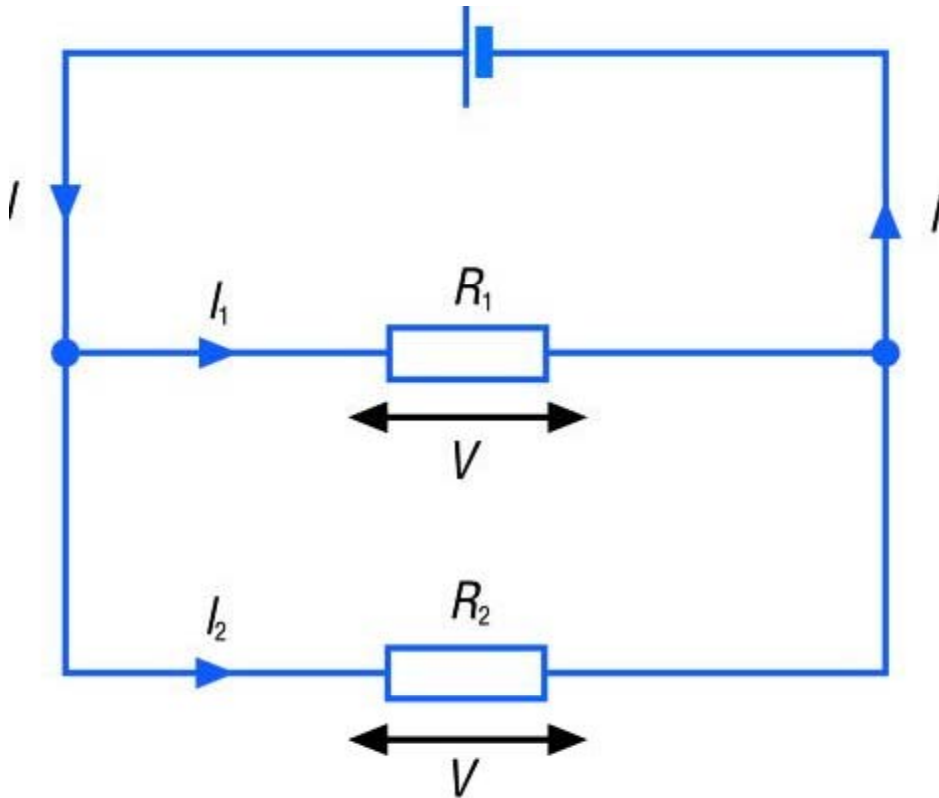An electrical circuit in which the components are connected side by side. The current flowing in the circuit is shared by the components.



Voltage:

$$V_T = V_1 = V_2$$

Resistance:

$$1/R_T = 1/R_1 + 1/R_2$$

Current:

$$I_T = I_1 + I_2$$

Ohm's Law

$$V=IR$$

One **amp** of current will flow through a resistance of one **ohm** if one **volt** of electrical force is applied to the circuit.

V=Volts

I=Amps

R=Ohms



Applying Ohm's Law

12 Volt Power Supply
24 Ω Resistor

V = 12 Volts
R = 24 Ohms

Then...

I = V/R
I = 12 / 24
I = 1/2 Amp



Applying Ohm's Law

Choosing an LED

$$R = V/I$$

Calculate Voltage:

$V_S =$ supply voltage = 9 Volts

$V_L =$ LED voltage = ~ 2V for Red LEDs

$V = (V_S - V_L) = (9V - 2V) = 7 \text{ Volts}$

Calculate Amperage:

$I =$ LED current = ~ 20mA = **.02A**

$$R = 7V / 0.02A$$

$$R = 350 \Omega$$

Any resistor equal or greater than 350Ω will work, but higher values will dim the LED more.

