

IAT 884

Alternate Output:

Motors, Movement, and Control Voltage

Motors

Types

Standard DC Motors

Speed of rotation is determined by supplied voltage

Servo

Alignment is set by a microcontroller from 0 – 180 degrees*

Stepper Motors

Precision Aligned using a microcontroller


Solenoids

Motors that have a forward and backward (linear) motion

*Servos can be modified to rotate 360 degrees

Motors

Types

 

Motors

Standard DC Motors

Operation

Speed of rotation is determined by supplied voltage

Motors are all rated for a specific voltage.

Do not exceed this voltage or you will burn out your motor.

Motor Concerns:

Motors produce a magnetic field that can generate back voltage in a circuit which can damage a microcontroller.


A motor may require a lot of voltage. The Arduino board can only output 5 volts.

Motors

Motors Concerns

Preventing Back Voltage

 When a motor's supply voltage is removed, it can **induce** a current ("back EMF" for the keepers) the wrong way through your circuit, causing damage to sensitive components. To prevent this you put a **Snubber Diode** (aka flyback, clamp, etc.) in your circuit.




Motors

Motor Concerns

Preventing Reverse (kick) Voltage

 A **Snubber Diode** is a diode placed inversely parallel to an inductive load. This provides an alternate path for the current and will protect your valuable microcontroller from surges.



Common Diodes:

1N4148

1N4001-1N4007

Motors

Motor Concerns

High Current/Voltage Loads

Sometimes a motor, light or other inductive load requires more voltage or current than a microcontroller can provide.

This requires 2 discrete power sources in a circuit.

The Microcontroller output voltage (0V-5V) can be used to proportionally change the voltage supplied to the motor (0V – 12V) by a separate power supply.

To do this we use a **transistor** (or relay).


Motors

Transistors

Transistors are used to switch or amplify voltage

A basic transistor has three connections, the **base**, the **collector**, and the **emitter**.

 There are many different kinds of transistors. Some look different, some act different. The two types of the most common (bipolar) transistors are **PNP** and **NPN**.



Transistors you might find in your kit:

- TIP120
- TIP122

Motors

Transistors

Transistors are used to switch or amplify voltage

NPN - Switch the **negative** side of a circuit by bringing the base **HIGH**

PNP - Switch the **positive** side of a circuit by bringing the base **LOW**

NPN = “**N**ever **P**oints **iN**”

PNP = “**P**oints **iN** **P**ermanently”



PNP



NPN

Motors

Transistors



Transistors are used to switch or amplify voltage

For our circuits we will almost always use NPN transistors.

The **Base** is connected to a control voltage (e.g. Microcontroller output)

The **Collector** is attached to the negative terminal of the motor (or light)

  The **Emitter** is connected to the common ground



NPN
Schematic
Symbol

Motors

Transistors



Transistors are used to switch or amplify voltage

The other type of transistor is the PNP transistor.

The **Base** is connected to a control voltage (e.g. Microcontroller output)

The **Collector** is attached to the positive terminal of the motor (or light)

  The **Emitter** is connected to the power source



Motors

Transistors

Transistors are used to switch or amplify voltage

IMPORTANT NOTE:



Transistors are fairly sensitive electronic components. The base can handle a limited current - typically 10-20 mA is safe and sufficient. BUT on certain types of transistors (e.g. MOSFET) it can be less than 5mA!!

Remember to use a current limiting resistor, just like with LEDs.


Motors

Transistors

Motor Control Circuit

  

NPN Schematic Symbol


 


Motors

Potentiometer

Variable Resistor

 
 
A potentiometer is a rotary voltage divider. It functions like a variable resistor changing the output voltage when the knob is turned.




Motors

Transistors

 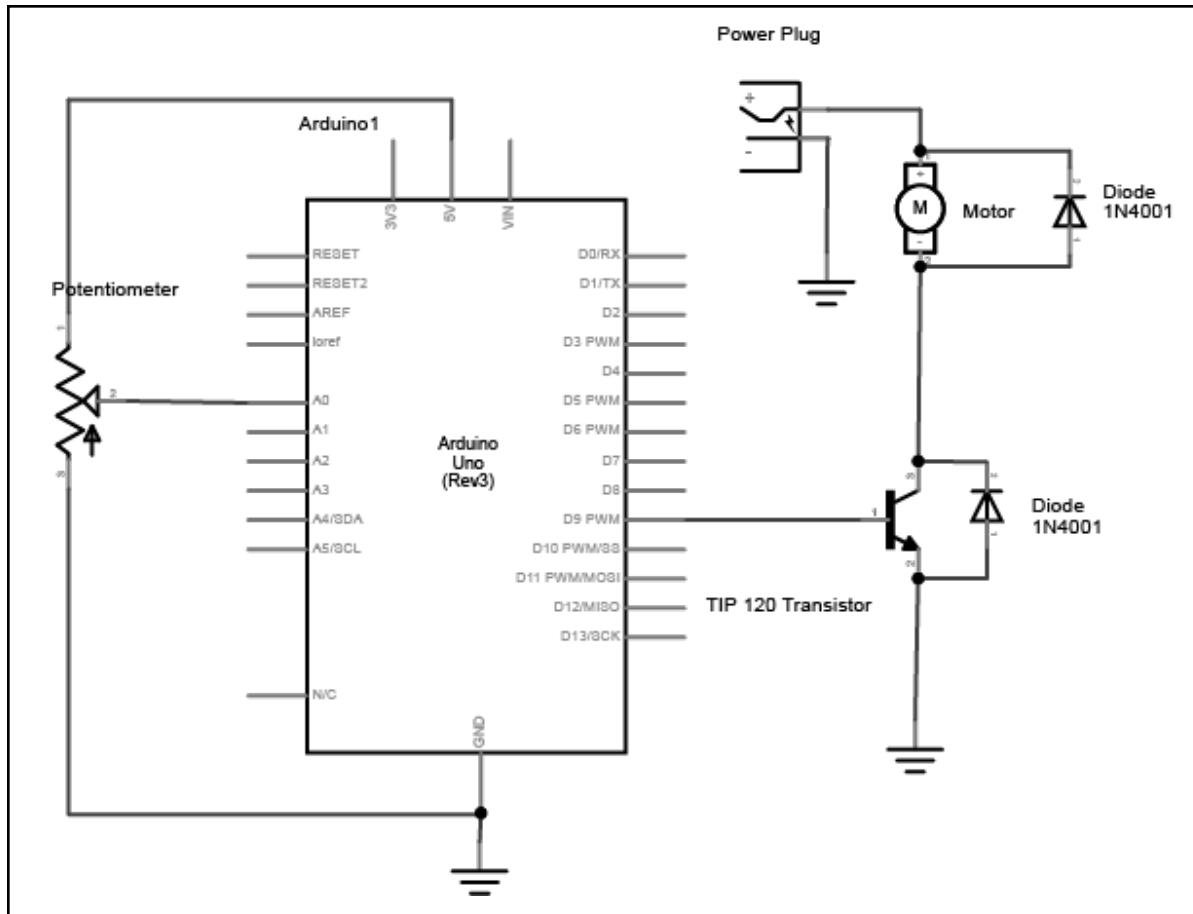Example: Use a potentiometer to control motor speed




NPN Schematic Symbol

 

Motors

Transistors

Arduino Circuit

 

Motors

Transistors

Example: Blink sketch to test motor

```
const int transistorPin = 9; // connected to the base of the transistor

void setup() {
  // set the transistor pin as output:
  pinMode(transistorPin, OUTPUT);
}

void loop() {
  digitalWrite(transistorPin, HIGH);
  delay(1000);
  digitalWrite(transistorPin, LOW);
  delay(1000);
}
```

Motors

Transistors

Example: Use a potentiometer to control motor speed

```
const int transistorPin = 9; // connected to the base of the transistor

void setup() {
  // set the transistor pin as output:
  pinMode(transistorPin, OUTPUT);
}


void loop() {
  // read the potentiometer:
  int sensorValue = analogRead(A0);
  // map the sensor value to a range from 0 - 255:
  int outputValue = map(sensorValue, 0, 1023, 0, 255);
  // use that to control the transistor:
  analogWrite(transistorPin, outputValue);
}
```

Motors

H-Bridge Circuits

Bidirectional Motor Control

 Transistors are great if we only need to move a motor in one direction. H-Bridge Circuits allow us to change a motor's direction on demand. An H-Bridge is just 4 transistors wired together.




H-Bridge Circuit

Motors

H-Bridge Circuits



Wiring Scheme

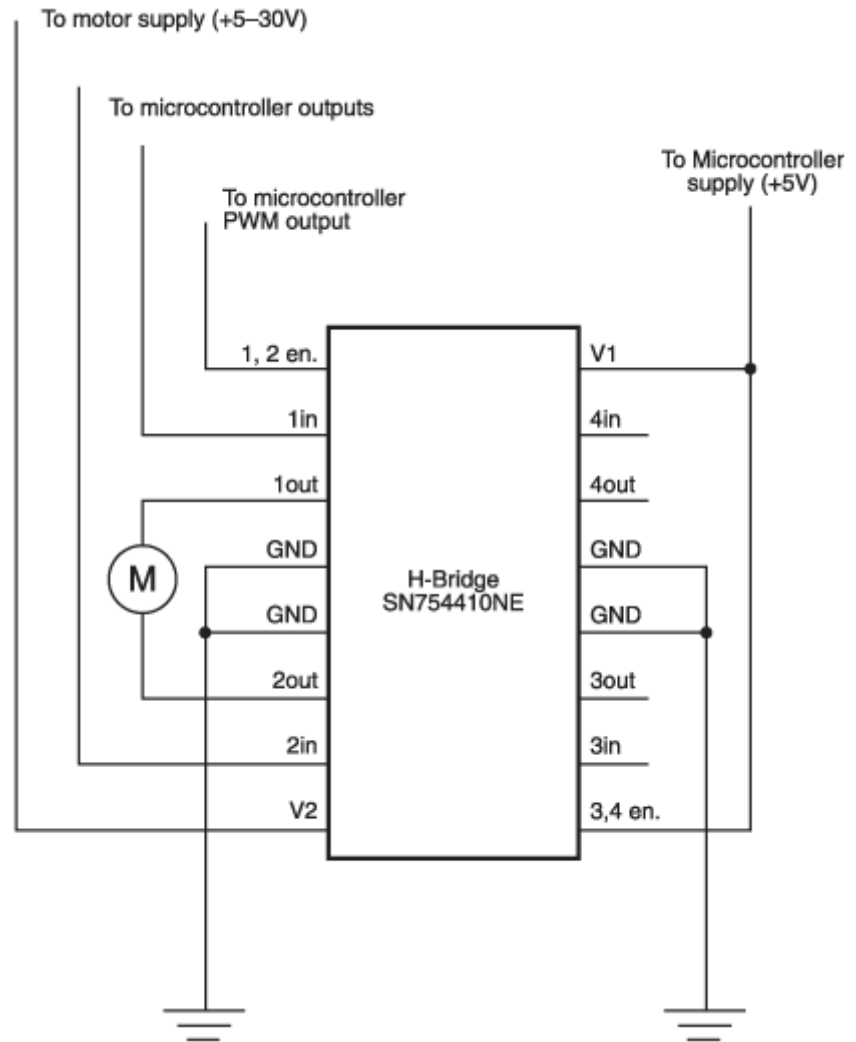

Motors

H-Bridge Circuits

Connecting to an Arduino

 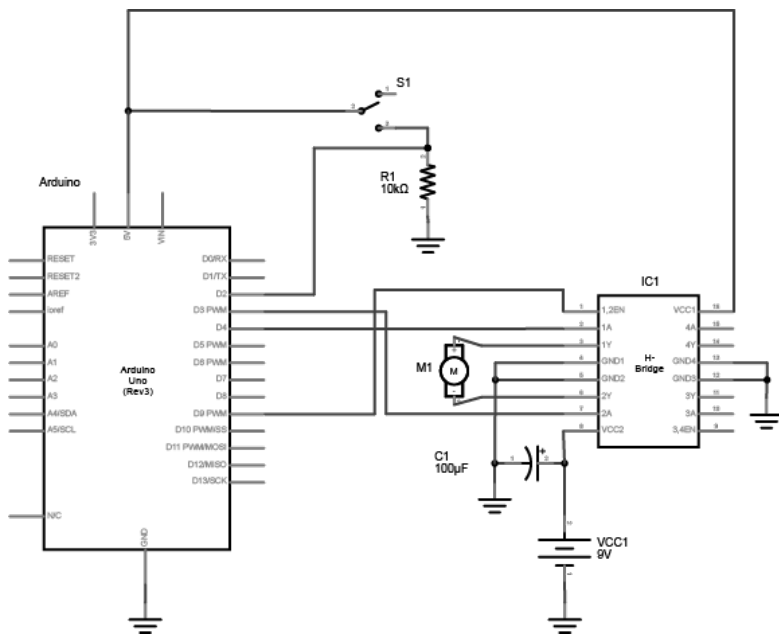



Motors

Voltage Regulators

Voltage regulators convert a higher voltage to a lower voltage.

They come in a variety of types including 3.3V, 5V and 9V.

  They can get HOT under normal operation, but this might also indicate that you have wired something incorrectly!



Regulators you might find in your kit:

- 7805CT
- LM1084

Motors

Servo Motors


Servo Motors Use Pulse coded modulation to change a motor's position from 0 -180. When a motor receives a specific pulse it will move to the corresponding angle and maintain that position as long as it continues to receive the same signal. The signal must be resent at least every 20 ms.

Pulse Length

1.5 ms 90 Degrees (Neutral)

> 1.5 = closer to 180 degrees

< 1.5 = closer to 0 degrees.

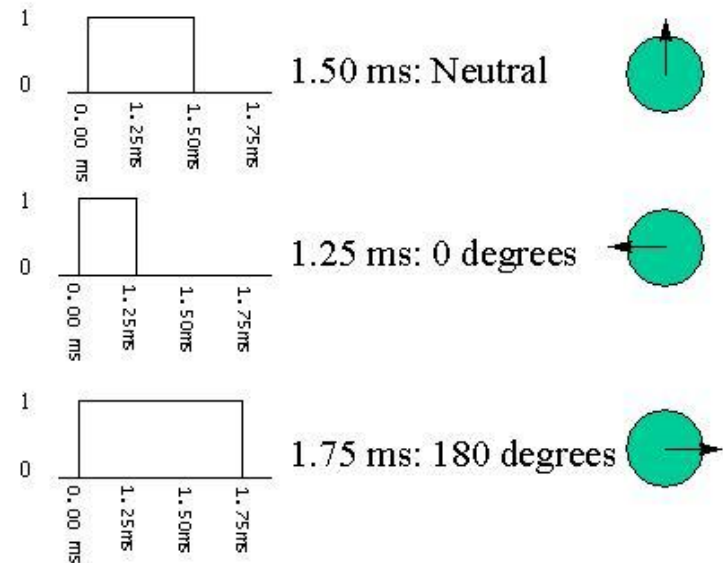

Motors

Servo Motors

Arduino

The Arduino programming language has two methods for controlling servos.

- 1. Manually set the pulse lengths, min pulse, max pulse, etc.**
- 2. Use the Software Servo library <servo.h> by Arduino Playground.**

Motors

Servo Motors

Servo.h – Main Functions

attach(int)

Turn a pin into a servo controller. Calls pinMode.

detach()

Release a pin from servo control.

write(int)

Set the angle of the servo in degrees, 0 to 180.

read()

return that value set with the last write().

attached()

return 1 if the servo is currently attached.

Motors

Servo Motors

Example: Control the position of a motor using a potentiometer

```
#include <Servo.h>
```

```
Servo myservo; // create servo object to control a servo
```

```
int potpin=0; // analog pin used to connect the potentiometer
```

```
int val; //variable to read the value from the analog pin
```

```
void setup(){
```

```
myservo.attach(9); //attaches the servo on pin 9 to the servo object Serial.begin(9600);
```

```
}
```

```
void loop(){
```

```
val = analogRead(potpin); // reads the value of the potentiometer
```

```
val = map(val, 0, 1023, 0, 180); //scales it to use with the servo (value between 0 and 180)
```

```
myservo.write(val); //sets the servo position according to the scaled value
```

```
Serial.println(val);
```


```
delay(15); //waits for the servo to get there
```

```
}
```

Motors

Servo Motors

 Example: Control the position of a motor using a potentiometer



Activities

Design a circuit that uses a potentiometer to control a DC Motor. You should use a battery as a separate power source for the motor and an NPN transistor to switch the current. You will need to use a voltage regulator to bring the voltage supplied to the motor down to 5v.

Step 1: Attach Potentiometer (and test functionality using serial window)

Step 2: Build Voltage Regulator circuit to power motor (test with multi-meter)

Step 3: Unplug from USB, finish circuit by adding transistor and motor elements.

Step 4: Attach AC adapter to Arduino Board to power

Design a circuit to control a servo motor. Use the potentiometer from your previous circuit to control the position of the servo. Use the AC adapter to power the Arduino board to ensure that you have enough power for the system and to make it more portable. *You can use the software servo library from Arduino Playground.*

Step 1: Make sure potentiometer is working and check output range.

Step 2: Convert incoming value from the potentiometer to a value between 0 – 180 to correspond to the angle of the servo

Step 3: Unplug from USB, and attach servo motor

Step 4: Attach AC adapter to Arduino Board to power