

IAT 884

Lab 6

Alternate Output: Motors and Actuation

Preparation:

READ: Hartman: CH. 8 (Motors)

READ (optional): Hartman: CH. 8 (Light & Sound)

READ (review): Essential Electronics Concepts - POWER! (on Wiki)

READ (review): Basic Components – Diodes, Transistors, & Relays (on Wiki)

Deprecated:

In *Programming Interactivity* Read:

A. [Motors](#) (p. 380 -391)

[Solenoids](#) (p. 417 – 420)

Resources

Servo Library:

<http://www.arduino.cc/en/Reference/Servo>

Transistor Basics:

<http://www.kpsec.freeuk.com/trancirc.htm>

Working with Transistors:

<http://www.kpsec.freeuk.com/components/tran.htm>

Controlling High Current Loads with a Transistor:

<http://itp.nyu.edu/physcomp/Tutorials/HighCurrentLoads>

H-Bridge Basics:

http://www.modularcircuits.com/h-bridge_secrets1.htm

Servo Motor Resources

<http://itp.nyu.edu/physcomp/Labs/Servo>

<http://www.arduino.cc/playground/ComponentLib/Servo>

<http://www.seattlerobotics.org/guide/servos.html>

<http://www.arduino.cc/en/Tutorial/Potentiometer>

In Class Activities:


Equipment:

Arduino
Servo Motor
DC Motor
12V AC Adapter
Power Plug
Voltage Regulator (5v)
Potentiometer
NPN Transistors (TIP 120)
Capacitors (1mf or 10mf)
Diode
Resistors (1k)
Wires
Breadboard


Heads Up!! Make sure that all your components share a common ground!!!! This is extremely important when using two power sources. You might blow a transistor or Arduino if you do not do this, but more likely, it just won't work.

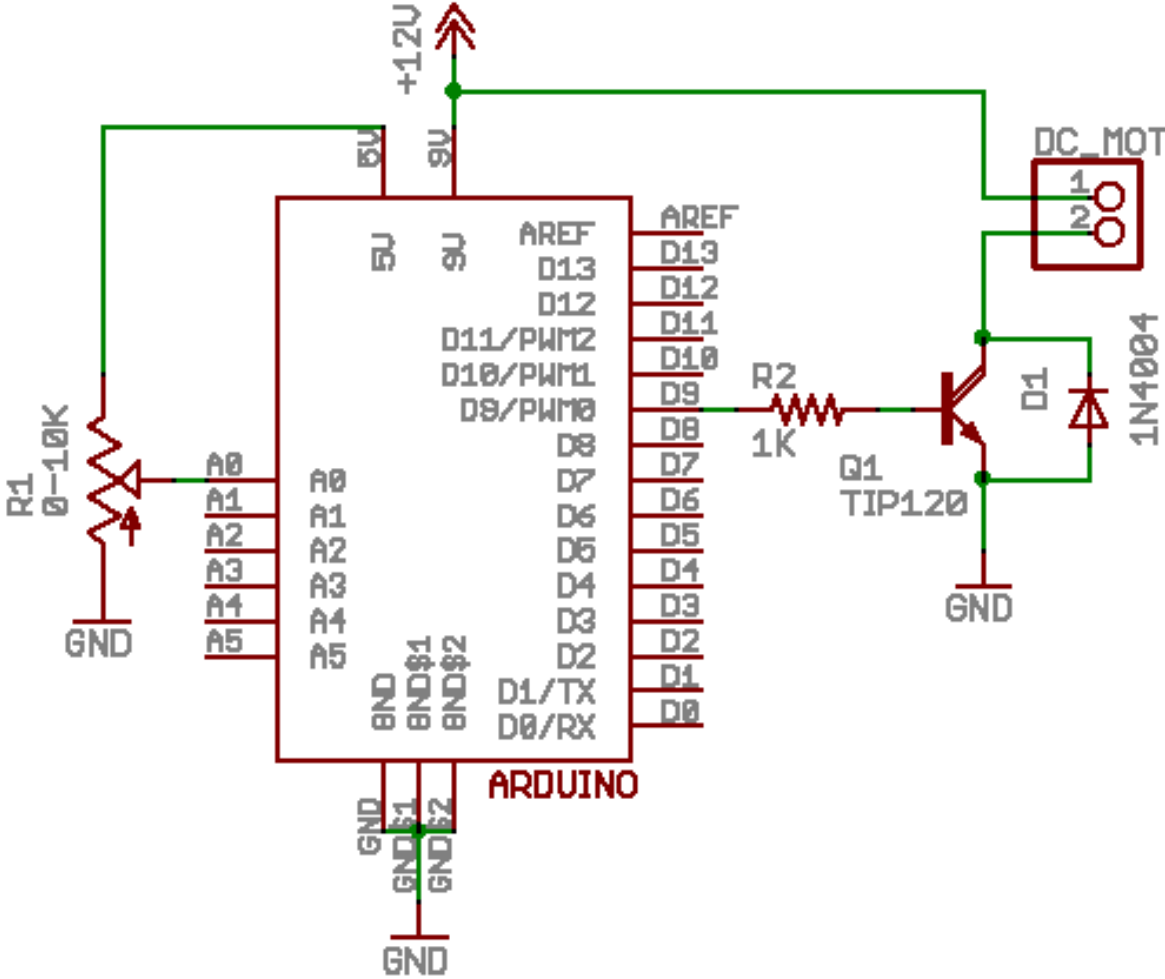- A. Design a circuit that uses a potentiometer to control a DC Motor. You need to use a 12 volt adapter as a separate power source for the motor and an NPN transistor to switch the current. You will need to use a voltage regulator to bring the voltage supplied to the motor down to 5v and a diode to prevent back current.
- *Step 1: Attach Potentiometer (and test functionality using serial window)*
 - *Step 2: Build Voltage Regulator circuit to power motor (test with multi-meter)*
 - *Step 3: Finish circuit by adding transistor, Diode, and motor elements.*
- B. Design a circuit to control a servo motor. Use the potentiometer from your previous circuit to control the position of the servo. Use the AC adapter to power the Arduino board to ensure that you have enough power for the system and to make it more portable. You can use the software servo library included with the Arduino software.
- *Step 1: Attach AC adapter to Arduino Board and adjust pin for external power.*
 - *Step 2: Make sure potentiometer is working and check output range.*
 - *Step 3: Convert incoming value from the potentiometer to a value between 0 – 180 to correspond to the angle of the servo [Map() function]*
 - *Step 4: Attach servo*

Schematic: Controlling DC motor speed using a potentiometer (MOVE DIODE)




NPN Transistor Usage

 


- Terminal Connections:**
- Base is connected to a control voltage (e.g. Microcontroller output)
 - The Collector is attached to the negative terminal of the load (e.g. motor or light)
 - The Emitter is connected to the common ground

 Illustrated DC Motor Circuit (Move diode to MOTOR instead – see TA)



The TIP 120 is a NPN transistor

 

Base to microcontroller
Emitter to ground
Collector to device

Diode from E to C when connected to inductive load like a DC motor

DC Motor Circuit Attached to an Arduino (This diode is correct!)

